 


7.11 Register files

A **three-state buffer** is a component that outputs $y = b$ if input a is 1, and outputs Z if a is 0. Z represents an electrical situation called **high impedance**. A wire with Z is akin to no wire. As such, three-state buffers support efficient combining of multiple wires. This will be seen when introducing register files below. Of course, only one connected wire can have a non- Z (0 or 1) value, else they will collide. Further details on three-state buffer and high impedance are beyond this material's scope.

Figure 7.11.1: Three-state buffer.



PARTICIPATION ACTIVITY

7.11.1: Three-state buffer.

Given a three-state buffer with control input a , data input b , and data output y .

1) If $a = 1$ and $b = 1$, then $y = ?$

- ☐ 1
- ☐ 'Z'

2) If $a = 1$ and $b = 0$, then $y = ?$

- ☐ 1
- ☐ 0

3) If $a = 0$ and $b = 0$, then $y = ?$

- ☐ 0
- ☐ 'Z'


A three-state buffer is more commonly called a **tri-state buffer**, but that name is trademarked. The term *three-state driver* (or *three-state output*) is also used.


An NxM **register file** efficiently implements access to N M-bit registers. A 16x32 register file has 16 registers, each 32 bits wide. Having 512 (16 times 32) wires connecting with those registers for loads, a register file consolidates loads through one 32-bit data output. Of course, the tradeoff is that only one register can be loaded at a time, as indicated by a 4-bit address input. Loading a register file is known as a **write** operation. The data input, address input, and load enable input for writing are together called a **write port**. A register file consolidates read wires into a single 32-bit data output, 4-bit address input, and enable input, forming a **read port**. A read port may use three-state buffers to efficiently connect the data wires.

PARTICIPATION ACTIVITY

7.11.2: 4x8 register file.

Start ☐ 2x speed

 

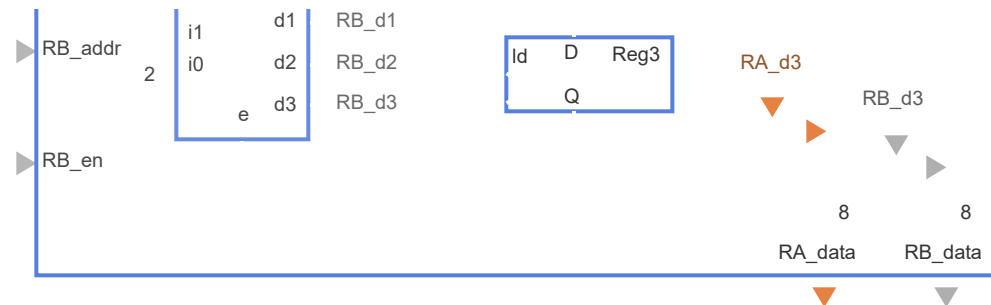

PARTICIPATION ACTIVITY

7.11.3: Register file.

- 1) A 32x8 register file consists of ____ registers.
 - ☐ 8
 - ☐ 32
 - ☐ 40
- 2) The write address, write enable control, and write data are collectively known as what?
 - ☐ Write port
 - ☐ Read port
 - ☐ Write decoder
- 3) W_en must be set to 1 to write to, or load, a register.
 - ☐ True

☐ False

4) Given a 32x8 register file, how many bits is W_addr?

☐ 2

☐ 3

☐ 5

5) Assuming a register file with one write port and two read ports, write and read operations can occur simultaneously.

☐ True

☐ False

6) Assuming a register file with one write port and two read ports, two read operations can occur simultaneously.


☐ True

☐ False

**PARTICIPATION
ACTIVITY**

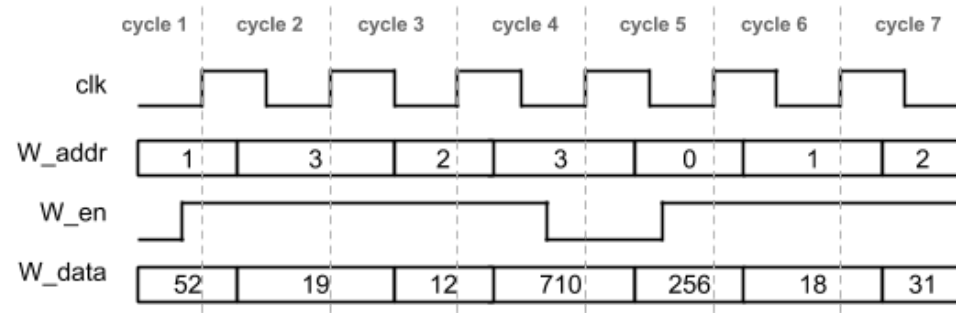7.11.4: Register files: Writing.

For the given values of W_addr, W_en, and W_data, indicate the register file's contents in a given clock cycle.



4x8 register file
(1 wr, 2 rd)

Reg0	?
Reg1	?
Reg2	?
Reg3	?

1) Reg1, cycle 2

Check

Show answer

2) Reg1, cycle 6

Check

Show answer

3) Reg3, cycle 5


Check

Show answer

PARTICIPATION ACTIVITY

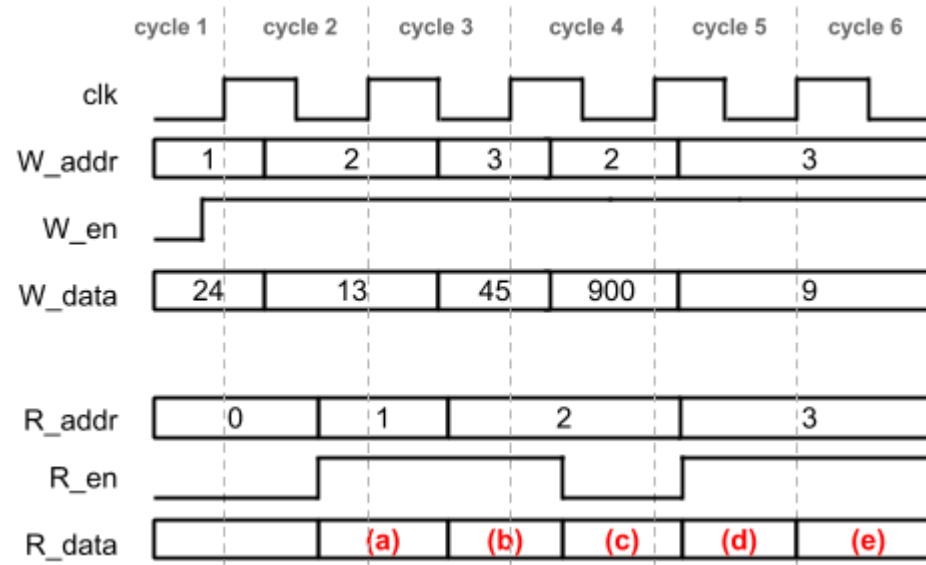7.11.5: Register files: Writing and reading.

Assume a 4x32 register file with one read port and one write port. Determine R_data's value at each indicated time. If appropriate, type: Z.



1) (a)

Check

[Show answer](#)

2) (b)

Check

[Show answer](#)

3) (c)

Check

[Show answer](#)

4) (d)

Check**Show answer**

5) (e)

Check**Show answer****CHALLENGE
ACTIVITY**

7.11.1: Register file writing and reading.

Start

Update the values after rising clk.

74

0

1

0

0

0

0

87

99

94

99

1

2

3

4

5

6

7

8

[Check](#)[Next](#)

 [Provide feedback on this section](#)