

## 7.8 Load registers

### Load register design

A designer may want to **load** a register only on certain clock cycles rather than on every clock cycle. Registers commonly have a control input named "load" or "ld". Implementing such a load register can be done using 2x1 muxes.


#### PARTICIPATION ACTIVITY

7.8.1: 3-bit load register implemented with 3 flip-flops and muxes.

Start

☐ 2x speed

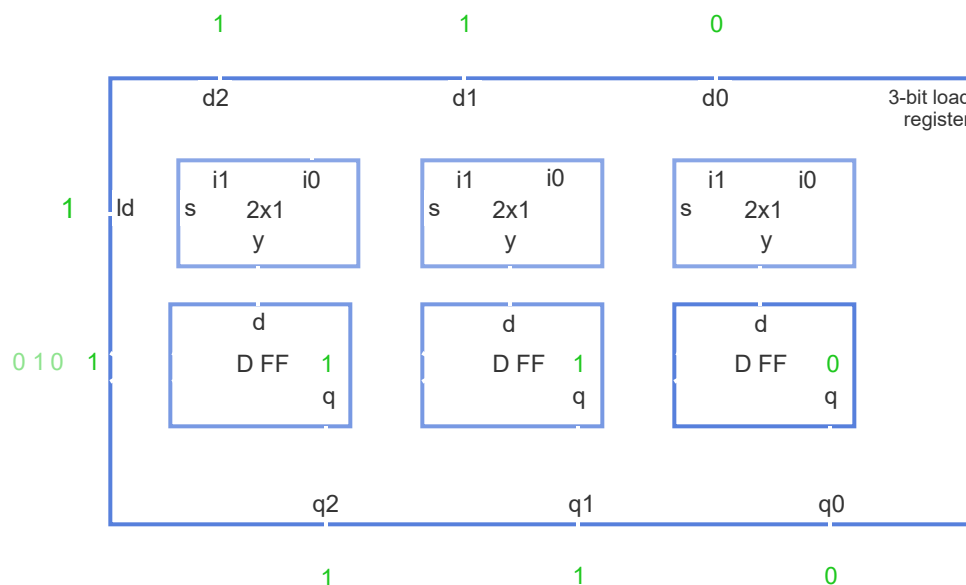
Note: clk connections with FF clk inputs are not shown.



#### Function table

ld	Register function
0	Maintain
1	Load

#### Block symbol

 

Many registers also come with a reset or clear input, to reset/clear the stored bits to 0's (described in another section).

### PARTICIPATION ACTIVITY

7.8.2: Multi-bit data in a timing diagram.

Start ☐ 2x speed

a


B(3) 

2	5	4	5
---	---	---	---

### PARTICIPATION ACTIVITY

 7.8.3: Trace a load register's behavior.

For the given values of D, ld, and clk, indicate the register's Q value.



1) (a)

Q =

Check

Show answer

2) (b)

Q = 

Check

Show answer

3) (c)

Q = 

Check

Show answer

4) (d)

Q = 

Check

Show answer

## Load register behavior

An N-bit **load register** (such as an 8-bit load register or just 8-bit register) stores N bit values, loading new bit values when a load input is 1. A load input (ld) indicates when the register should be loaded. A reset input (rst) may exist that indicates register's bits should be reset to 0 (having priority over ld).


All a circuit's registers may share one **clock** signal, whose **rising edge** (the instant a 0 changes to 1) synchronizes loading c (like a drum beat synchronizes a marching band).

PARTICIPATION  
ACTIVITY

7.8.4: Registers.

Start

☐ 2x speed

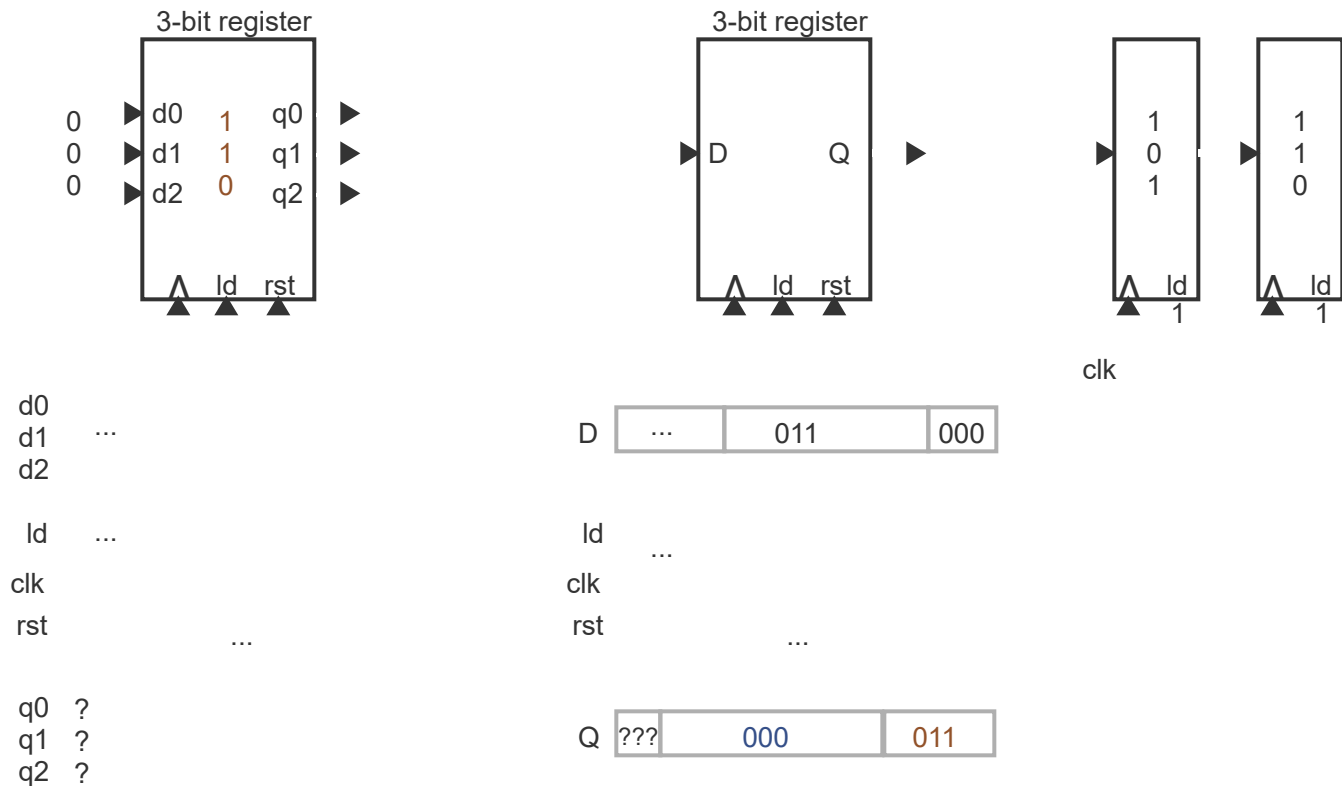

### PARTICIPATION ACTIVITY

#### 7.8.5: Registers.

Consider the above 3-bit load register.

- 1) What are q2q1q0 when rst = 1 and ld = 1, assuming q2q1q0 were previously 110, and d2d1d0 are 111?

☐ 110

☒ 000

☐ 111

☐ Depends on clk's value

2) Assume rst = 0, ld = 1, d2d1d0 are 110, and q2q1q0 are 111. When a rising clock occurs, what do q2q1q0 become?

☐ 111

☐ 110

☐ 000

3) Assume rst = 0, ld = 0, d2d1d0 are 110, and q2q1q0 are 111. When a rising clock occurs, what do q2q1q0 become?

☐ 111

☐ 110

☐ 000

4) Assume Y connects to register R1's inputs, and R1's outputs connect to R2's data inputs. On rising clock 1, Y was 100. On rising clock 2, Y was 000. On rising clock 3, Y was 111. What is now in R2?

☐ 100



☐ 000

☐ 111

**CHALLENGE  
ACTIVITY**

7.8.1: Indicate Z's value over time.

Start

  

1	2	3	4	5	6
---	---	---	---	---	---

[Check](#)[Next](#)

 [Provide feedback on this section](#)