

4.3 Comparators


A **comparator** compares two numbers, indicating whether the numbers are equal, or which number is greater. Same-length numbers can be compared by hand just like base ten numbers: Starting from the left, digits are compared until a difference

PARTICIPATION ACTIVITY

4.3.1: Comparator.

Start ☐ 2x speed

0 1 0 1 0 1 0 1

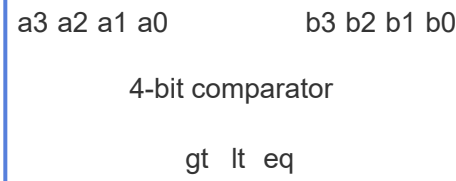

Note: A is a3a2a1a0. B is b3b2b1b0.

A: 0101(5)

A's bit is 0, B's bit is 1.

A < B

B: 0111(7)

A: 0100(4)

A's bit is 1, B's bit is 0.

A > B

B: 0010(2)

A: 0101(5)

A's bits are the same as B's bits.

A = B

B: 0101(5)

PARTICIPATION ACTIVITY

4.3.2: Comparator.

Indicate which comparator output will be 1.

1) A: 1100

B: 1101

☐ gt☐ lt☐ eq

2) A: 0100

B: 1000

☐ gt☐ lt☐ eq

3) A: 1111

B: 1111

☐ gt☐ lt☐ eq

A **carry-ripple comparator** compares two N-bit numbers from left to right, with the result of each digit's comparison "rippling" digit. For each digit, a **one-bit comparator** compares two bits a and b only if the eq input was 1 from the higher digit, else just a gt 1 or an lt 1. The rightmost digit's output becomes the N-bit comparator's output. The name "carry-ripple" refers to the comparator's implementation to a carry-ripple adder's implementation.

**PARTICIPATION
ACTIVITY**

4.3.3: Carry-ripple comparator.

Start ☐ 2x speed


0 1 0 1

0 1 1 1

a3 a2 a1 a0

4-bit comparator

b3 b2 b1 b0

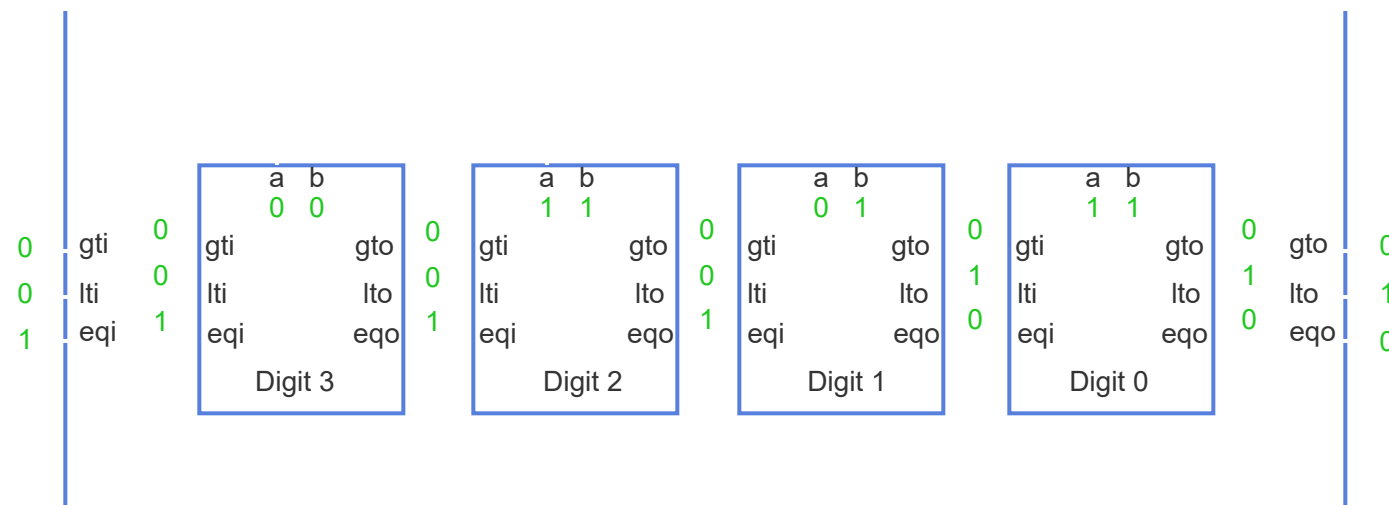

The correct output of leftmost digit ripples to next digit, and so on. Eventually the external outputs become correct.

PARTICIPATION ACTIVITY

4.3.4: Carry-ripple comparator.

Consider a 4-bit carry-ripple comparator (seen in the above animation). Indicate which output will be 1 for each digit.

Assume: $a_3a_2a_1a_0 = 0100$ (4), $b_3b_2b_1b_0 = 0010$ (2)

1) Digit 3

- ☐ *gto*
- ☐ *lto*
- ☐ *eqo*

2) Digit 2

- ☐ gto
- ☐ lto
- ☐ eqo

3) Digit 1

- ☐ gto
- ☐ lto
- ☐ eqo


4) Digit 0

- ☐ gto
- ☐ lto
- ☐ eqo

A one-bit comparator can be implemented using combinational logic for each output. A designer could start by filling in a truth table with inputs gt_i , lt_i , eq_i , a , and b , and 3 outputs gto , lto , eqo . The truth table will have $2^5 = 32$ rows. Alternatively, the designer can use logic equations.

- eqo should be 1 if eq_i is 1 AND a , b are the same. Thus: $eqo = eq_i(ab + a'b')$.
- gto should be 1 if gt_i is 1, OR eq_i is 1 AND ab are 10. Thus: $gto = gt_i + eq_i(ab')$.
- lto should be 1 if lt_i is 1, OR eq_i is 1 AND ab are 01. Thus: $lto = lt_i + eq_i(a'b)$.

Figure 4.3.1: 1-bit comparator circuit (used in questions below).

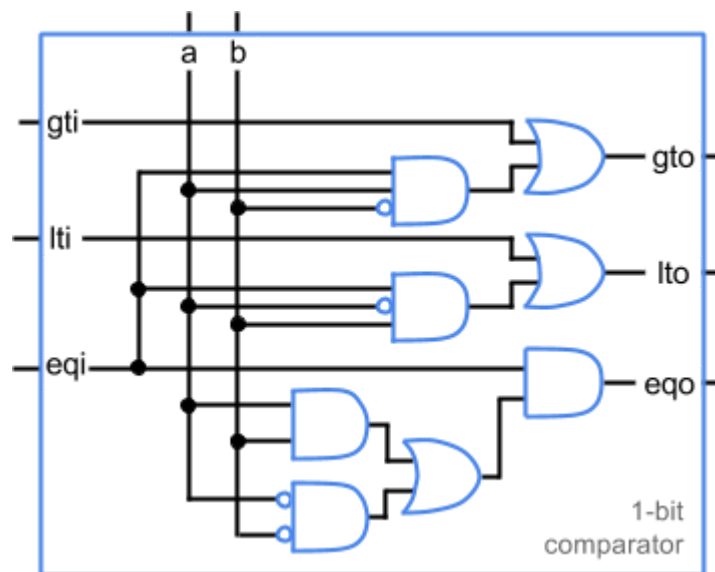**PARTICIPATION
ACTIVITY**

4.3.5: 1-bit Comparator.

1) Given: $a = 1$, $b = 1$, $gti = 0$, $lti = 0$, $eqi = 1$.

☐ $eqo = 0$

☐ $eqo = 1$

2) Given: $a = 1$, $b = 0$, $gti = 0$, $lti = 0$, $eqi = 1$.

☐ $eqo = 0$

☐ $eqo = 1$

3) Given: $a = 0$, $b = 0$, $gti = 0$, $lti = 1$, $eqi = 0$.

☒ eqo = 0

☐ eqo = 1

4) Given: a = 0, b = 0, gti = 0, lti = 1, eqi = 0.

☐ lto = 0

☐ lto = 1

5) Given: a = 0, b = 1, gti = 0, lti = 0, eqi = 1.

☐ lto = 0

☐ lto = 1

6) Given: a = 1, b = 0, gti = 0, lti = 0, eqi = 1.

☐ lto = 0

☐ lto = 1

7) Given: a = 0, b = 1, gti = 1, lti = 0, eqi = 0.

☐ gto = 0

☐ gto = 1

 [Provide feedback on this section](#)