

7.19 Base MIPSzy + slt

A designer can extend the base MIPSzy to support the slt instruction. The designer might first modify the behavioral description opcode 000000 and function code 101010, with the actions being to set the first operand register with 1 if second register < third, else setting the first register with 0.

The designer can then modify the processor circuit to carry out those actions. The designer can extend the ADD component input signal indicating that the component should perform a less-than comparison rather than an addition, outputting 1 if input A < input B, else outputting 0 (the 1 and 0 are actually 32 bits: 00..01 and 00..00). Because the component now does more than just addition, the designer might name the component ALU. An **ALU (arithmetic-logic unit)** is a combinational component that performs arithmetic and logic operations needed by a processor, like add, subtract, compare, AND, etc. This ALU only does add and compare.

Finally, the designer would update the control logic to feed the two RF registers to the ALU and set alu_less = 1, and write the result to the RF (the paths for those reads and write already exist to support the very similar add instruction).

PARTICIPATION ACTIVITY

7.19.1: Creating a circuit of components that supports the MIPSzy behavioral description's actions.

Start ☐ 2x speed


```

ir = IM[PC/4];
PC = PC + 4;
// Assume ir31_26... extracted
// lw
if (ir31_26 == 0b100011) {
    ...
}
// sw
else if (ir31_26 == 0b101011){
    ...
}
// addi
else if (ir31_26 == 0b001000){
    ...
}
// add
else if ((ir31_26 == 0b000000)
        &&(ir5_0 == 0b100000)){

```

ALU

less

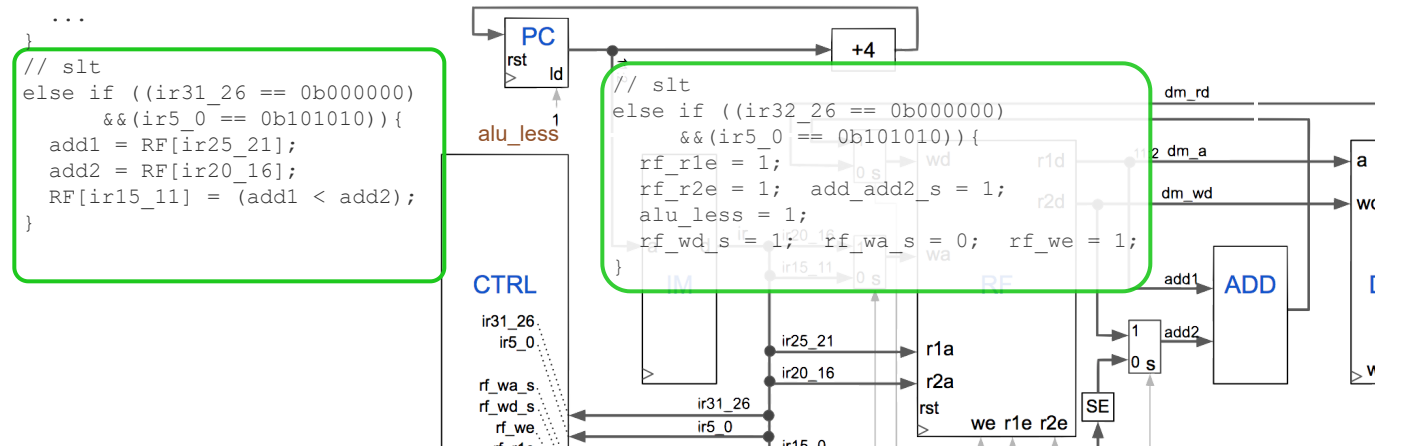

PARTICIPATION ACTIVITY

7.19.2: Extending the base MIPSzy to support the `slt` instruction.

- 1) If `add1` is less than `add2`, what does the ALU output? Type one digit.

Check

Show answer

- 2) The control logic actions for `slt` are nearly identical to those for `add`. Type the statement that was added for `slt`.

Check

Show answer

- 3) If `add1` is not less than `add2` (being equal or greater), a 0 will be written into the register specified by which `ir` bits? Type answer as: `ir5_0`

Check**Show answer****CHALLENGE
ACTIVITY**

7.19.1: slt extension in MIPSzy.

Start

1

Enter the bits for each item if \$t5 = 7 and

2

asm: slt \$t4, \$t5, \$t2

ir: 000000 01101 01010 01100 101010
 \$t5 \$t2 \$t4

Ex: 110010

Ex: 110010

Ex

