


3.8 Tradeoffs

A particular desired behavior, like adding two 4-bit numbers, may have alternative circuit implementations. A **tradeoff** is a design decision that improves one implementation metric while worsening another. An implementation **metric** is a measurement of an implementation's goodness. A common circuit metric is a circuit's size, with smaller size being better. Another is circuit delay, with less delay being better. Unfortunately, decreasing size usually increases delay, representing a tradeoff. Other common metrics include power and cost.

In contrast to a tradeoff, a design decision that improves some metric(s) without worsening any others is called an **optimization**.

PARTICIPATION ACTIVITY

 3.8.1: A behavior may have alternative implementations that trade off size and delay.



PARTICIPATION ACTIVITY

3.8.2: Tradeoffs.

Consider implementing a particular behavior. Indicate whether implementation B is a tradeoff compared to implementation A. (Units are intentionally omitted for this generic example).

- 1) A's size is 100, delay is 2.
B's size is 60, delay is 4.

- ☐ Tradeoff
☐ Not a tradeoff

- 2) A's size is 100, delay is 2.
B's size is 80, delay is 2.

- ☐ Tradeoff
☐ Not a tradeoff

Multiple approaches exist for determining circuit size. One approach estimates transistors, assuming every gate input requires two transistors, and ignoring inverters for simplicity. A 2-input gate requires $2 \text{ inputs} \cdot 2 \text{ trans/input} = 4$ transistors. A 3-input gate requires 6 transistors. A 4-input gate requires 8 transistors.

Wires also contribute to size, but ignoring wires as above is a common approximation.

Although each gate may have a unique delay and wires also have delay, a quick approach for approximating circuit delay is the number of gates from a circuit's inputs to output, known as **gate delays**. Inverters are ignored for simplicity.

If multiple paths exist from inputs to output, the circuit's delay is the longest path, called the circuit's **critical path**.

Real gates have differing delays. A 3-input gate has slightly longer delay than a 2-input gate. Wires also have delay. But counting gates as above is a common approximation.

**PARTICIPATION
ACTIVITY**

3.8.3: Circuit size and delay.

Determine size in units of transistors, and delay in units of gate-delays.



(a)



(b)



(c)

1) Size of (a)

transistors

Check

[Show answer](#)

2) Size of (b)

transistors

Check

[Show answer](#)

3) Size of (c)

transistors

Check

[Show answer](#)

4) Delay of (b)

gate-delays

Check

[Show answer](#)

5) Delay of (c)

gate-delays

Check

[Show answer](#)

Size and delay can be estimated directly from an equation. Ex: $y = abc + def$ has a 3-input AND for abc , another 3-input AND input OR, so size is $3 \cdot 2 + 3 \cdot 2 + 2 \cdot 2 = 16$ transistors. The circuit has a column of AND gates followed by an OR, so delay is 2

**PARTICIPATION
ACTIVITY**

3.8.4: Estimating size and delay from an equation.

- 1) $y = a$. Size = ____ transistors?
☐ 0
☐ 2
- 2) $y = ab$. Size = ____ transistors?
☐ 4
☐ 8
- 3) $y = ab + bc$. Size = ____ transistors?
☐ 8
☐ 12
- 4) $y = ab + bc$. Delay = ____ gate-delays?
☐ 1
☐ 2
- 5) $y = a'b'$. Size = ____ transistors?
☐ 4
☐ 6
- 6) $y = ab + a'b'$. Delay = ____ gate-delays?
☐ 2
☐ 3

7) $y = a + bcd$. Size = ____ transistors?

- ☐ 10
- ☐ 12

8) $y = a + b + cd$. Size = ____ transistors?

- ☐ 10
- ☐ 12

 **Provide feedback on this section**