

7.6 SR latches

Storing a bit


A **sequential circuit**'s output is dependent on the present and the past *sequence* of input values, which necessarily means it stores at least one bit. In contrast, a **combinational** circuit's output is dependent only on the present *combination* of input values.

The following system stores a bit to control a lamp.

PARTICIPATION ACTIVITY

7.6.1: A lamp controlled by on and off buttons stores a bit to remember whether keep the lamp on or off.

Start ☐ 2x speed

 

PARTICIPATION ACTIVITY

7.6.2: Lamp that stores a bit.

Consider the example above.

- 1) When the On button is pressed, what value should be stored in the lamp?
 - ☐ 0
 - ☐ 1
- 2) When the On button is pressed and then released, what value should be stored in the lamp?
 - ☐ 0
 - ☐ 1
- 3) Suppose a user pressed On and released, then pressed Off and released. What should be stored in the lamp?
 - ☐ 0
 - ☐ 1
- 4) Without knowing any history of the button presses, a designer observes that neither button is currently being pressed. Does the designer know whether the lamp should be illuminated?
 - ☐ Yes
 - ☐ No

SR latch

The simplest circuit for storing a bit is called a **latch**. An **SR latch** stores one bit, with an input *s* to set the latch to 1, an input *r* to reset the latch to 0, and with the stored bit appearing on output *q*. *S* and *s* are for "set", and *R* and *r* for "reset".

Below is a circuit for an SR latch. Reminder: NOR outputs 0 if any input is 1.

PARTICIPATION ACTIVITY

7.6.3: An SR latch stores a bit.

Start ☐ 2x speed

0 s



0 r



q 0

Reminder

a	b	NOR
0	0	1
0	1	0
1	0	0
1	1	0

Timing diagram

s 1
0
r 1
0
q 1
0

Figure 7.6.1: SR latch behavior.

s	r	q
0	0	Previously-stored bit
0	1	0 ("Reset")
1	0	1 ("Set")
1	1	Unknown

**PARTICIPATION
ACTIVITY**

7.6.4: SR latch.

Indicate q's present value for the given input sequence. "s: 0..1" means s was 0 and is presently 1.

1) s: 0

r: 1

☐ 1

☐ 0

2) s: 0..0

r: 1..0

☐ 1

☐ 0

3) s: 0..0..1

r: 1..0..0

☐ 1

☐ 0

4) s: 0..0..1..0
r: 1..0..0..0

☐ 1

☐ 0

5) s: 0..0..1..0..1
r: 1..0..0..0..0

☐ 1

☐ 0


SR = 11 is problematic

s = 1 and r = 1 causes a problem. The 1's cause the NOR gates to output 0's. When s and r return to 0's, then both gates output 1's propagate back to the gate inputs, causing the gates to output 0's. Those 0's propagate back, causing 1's again. No bit value instead the latch oscillates. **Oscillate** means to change from 0 to 1 to 0 to 1 repeatedly. Due to different gate and wire delay the latch will settle into a stored 0 or 1, but which one is unknown.

PARTICIPATION ACTIVITY

7.6.5: SR latch problem: sr = 11 doesn't store a bit and will cause oscillation.

Start ☐ 2x speed

 

a	b	NOR
0	0	1
0	1	0
1	0	0
1	1	0

q 0 1 0 1

Timing diagram

s 1
0
r 1
0
q 1
0

**PARTICIPATION
ACTIVITY**7.6.6: SR latch when $s = 1, r = 1$.

1) Setting s and r to 1's simultaneously initially sets q to 1.

- ☐ True
☐ False

2) q oscillates while s and r are both 1's.

- ☐ True
☐ False

3) If s and r are both 1's, and then both change to 0's, q may oscillate.

- ☐ True
☐ False

SR latches are uncommon

SR latches were previously common when gates were expensive. But with gates far

cheaper (and smaller) today, the more robust D latch (discussed later), which extends an SR latch, is more common.


Example: Lamp with on/off buttons

The earlier lamp example can be implemented using an SR latch.

PARTICIPATION ACTIVITY

7.6.7: Lamp with on/off buttons implemented using an SR latch.

Start ☐ 2x speed

 

PARTICIPATION ACTIVITY

7.6.8: Lamp implemented using an SR latch.

Consider the example above.

1) While the On button is being pressed, does the lamp illuminate?

- ☐ Yes
☐ No

☐ Oscillates

2) If the On button is pressed and then released, does the lamp stay illuminated?

☐ Yes

☐ No

☐ Oscillates

3) If the user presses both On and Off buttons and then releases both of them, does the lamp illuminate?

☐ Yes

☐ No

☐ May oscillate

 **Provide feedback on this section**