

4.2 Subtractors


A **subtractor** computes $A - B$, where A and B are N -bit numbers, such as 8-bit numbers. If numbers are represented using two's complement representation, a subtractor can be built using an adder. Inverting B 's bits and setting the adder's carry-in to 1 adds B 's complement.

PARTICIPATION ACTIVITY

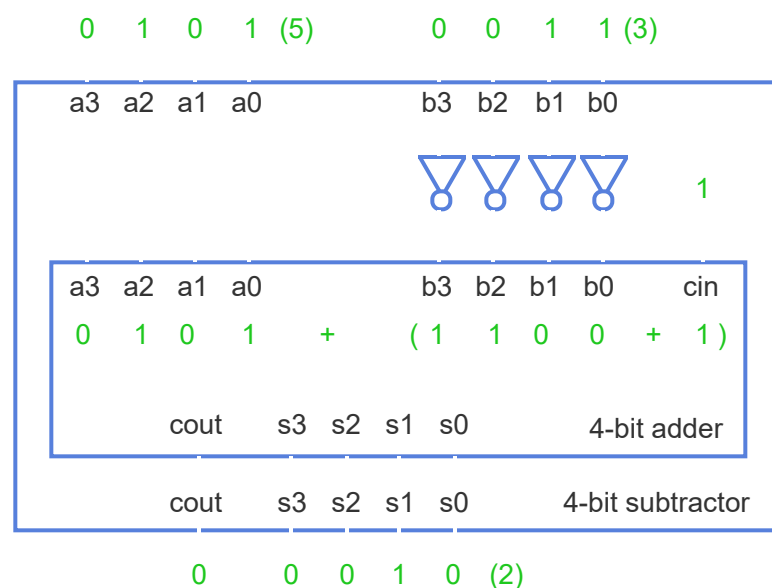4.2.1: A 4-bit subtractor.

Start ☐ 2x speed


Note: A is $a_3a_2a_1a_0$. B is $b_3b_2b_1b_0$.



$A - B$ is $A + (-B)$
 $a_3a_2a_1a_0 - b_3b_2b_1b_0$

$$\begin{aligned}
 5 - 3 &= 5 + (-3) \\
 &= 0101 + ((0011)' + 1) \\
 &= 0101 + (1100 + 1) \\
 &= 0010
 \end{aligned}$$

Block symbol

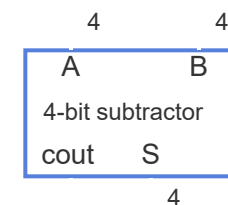

**PARTICIPATION
ACTIVITY**

4.2.2: Subtractor.

- 1) An adder can be used to perform subtraction if input B is represented in two's complement.
- ☐ True
- ☐ False
- 2) For a subtractor built from an adder, the adder is configured to subtract by setting the adder's cin bit to ____.
- ☐ 0
- ☐ 1
- 3) To perform $7 - 2$ using a 4-bit subtractor, A is 0111 and B is ____.
- ☐ 0010
- ☐ 1110

Because two's-complement representation performs subtraction by complementing and adding, a single adder circuit can add or subtract, thus saving circuit size.

**PARTICIPATION
ACTIVITY**

4.2.3: A 4-bit adder/subtractor.


Start ☐ 2x speed

Note: A is a3a2a1a0. B is b3b2b1b0.

0 1 0 1 0 0 1 1

sub = 0: addition

4.2. Subtractors

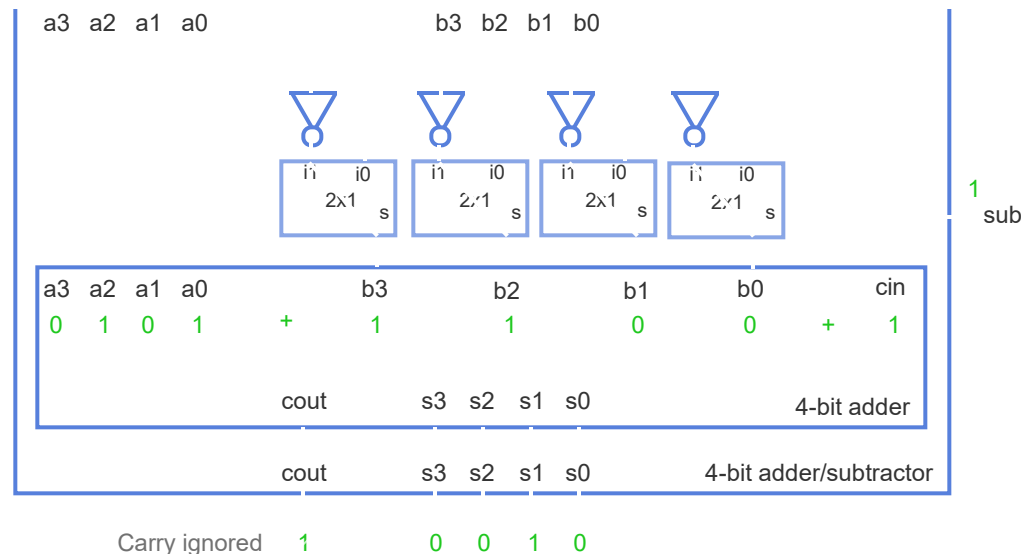

0011 (3) + 0100 (4)

0111 (7)


sub = 1: subtraction

0101 (5) - 0011 (3)

0101(5) + 1101 (-3)

0010 (2)

Block symbol

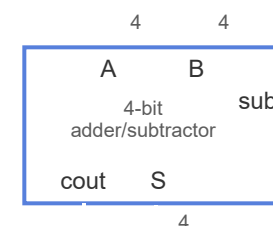PARTICIPATION
ACTIVITY

4.2.4: Adder/subtractor.

Consider a 4-bit adder/subtractor (seen in the animation above).

1) If sub is 0, what is the adder/subtractor component configured to do?

- ☐ Addition
- ☐ Subtraction
- ☐ sub does not determine the circuit's operation.

2) Which of the following operations are

not valid?

- ☐ 5 - 3
- ☐ (-5) - (-3)
- ☐ -5 + 3
- ☐ None of the above.

3) Configure the adder/subtractor to perform the following operation: $7 - 2$

- ☐ $a_3a_2a_1a_0 = 0111$
 $b_3b_2b_1b_0 = 0010$
 $sub = 0$
- ☐ $a_3a_2a_1a_0 = 0111$
 $b_3b_2b_1b_0 = 0010$
 $sub = 1$
- ☐ $a_3a_2a_1a_0 = 0010$
 $b_3b_2b_1b_0 = 0111$
 $sub = 1$

 **Provide feedback on this section**