

## 3.25 Combinational logic (Verilog)


In Verilog, a **module** defines a new component. A module definition starts with the module name, and a list of the module's named input or output of a module. Each module input and output must also appear in an input or output declaration.

### PARTICIPATION ACTIVITY
 
#### 3.25.1: DoorOpenDetector module definition.

Start ☐ 2x speed


```
module DoorOpenDetector (b, c, z) ;  
    input b, c;  
    output reg z;  
  
    // Module description goes here  
  
endmodule
```



### PARTICIPATION ACTIVITY
 
#### 3.25.2: Module definitions.

Match the module definition to the appropriate circuit.



(B) (A) (D) (C)

```
module DetectActivity(f, g, h);
  input f;
  output reg g, h;
  ...
endmodule
```

```
module DetectActivity(f, g, h);
  input f, g;
  output reg h;
  ...
endmodule
```

```
module OutputDisplay(f, g, h);
  output reg f, g, h;
  ...
endmodule
```

```
module OutputDisplay(f, g, h);
  input f, g;
  output reg h;
  ...
endmodule
```

Reset

A designer can describe a combinational circuit's function using an always procedure. An **always procedure** defines a state that executes throughout simulation. An always procedure's **sensitivity list** defines the inputs and variables whose value change causes the procedure to execute. A combinational circuit is sensitive to all of the circuit's inputs.

**begin** and **end** surround an always procedure's statements.

**PARTICIPATION  
ACTIVITY**

3.25.3: Always procedure describing a combinational circuit.

Start ☐ 2x speed

```
module DoorOpenDetector(b, c, z);  
    input b, c;  
    output reg z;  
  
    always @(b, c) begin  
        z = b & ~c;  
    end  
  
endmodule
```



**PARTICIPATION  
ACTIVITY**

3.25.4: Always procedures for combinational circuits.

Complete the always procedure for the provided combinational equations.

1)  $z = ab$

```
module GetSensorReading(a, b,
z);
    input a, b;
    output reg z;

    [ ] @(a, b) begin
        z = a & b;
    end
endmodule
```

[Check](#)[Show answer](#)

2)  $m = j'$   
 $n = jk$

```
module UpdateDisplay(j, k, m,
n);
    input j, k;
    output reg m, n;

    always @( [ ]) begin
        m = ~j;
        n = j & k;
    end
endmodule
```

[Check](#)[Show answer](#)

3)  $t = v's'm'$

```

module SetTimer(s, t, m, v);
    input v, s, m;
    output reg t;

    always @(s, ) begin
        t = ~s & ~v & ~m;
    end
endmodule

```

[Check](#)[Show answer](#)

4)  $m = f$   
 $q = f'$   
 $p = f'$

```

module GetSensorReading(f, m,
p, q);
    input f;
    output reg m, p, q;

     begin
        m = f;
        q = ~f;
        p = ~f;
    end
endmodule

```

[Check](#)[Show answer](#)

An **assignment statement** like  $y = a \& b$  assigns the left-side variable with the result of the right-side expression. A **variable** with the value being updated by assignment statements, and is declared using the reg keyword. An output can be declared in: `output reg y;`

An **expression** is a combination of items, like inputs, variables, literals, and operators, that evaluates to a value. Ex:  $a \& b$ , with bitwise AND operator. If  $a$  is 0 and  $b$  is 1, then the expression evaluates to  $0 \& 1$ , which is 0.

An operator is a symbol for a built-in calculation like  $\&$  for AND. **Bitwise operators** perform the specified Boolean operation on the operands.

Table 3.25.1: Bitwise operators.

Operator	Description
$\&$	Bitwise AND operation.
$ $	Bitwise OR operation.
$\sim$	Bitwise NOT operation.
$\wedge$	Bitwise XOR operation.
$\wedge \sim$	Bitwise XNOR operation.

**PARTICIPATION  
ACTIVITY**

3.25.5: Boolean expression in Verilog.

Directly convert each given Boolean expression to Verilog.

*Note: This activity requires answers that directly match the given expressions. Ex: For  $ab$ , type  $a \& b$ . Variations like  $b \& a$  are not accounted for.*

1)  $z = a + b$

$z =$    $;$

**Check**

**Show answer**

2)  $z = a'b$

$z =$    $\& b;$

Check

Show answer

3)  $z = (ab) + c$

$z =$    $;$

Check

Show answer

4)  $z = (ab') + (ac)$

$z =$    $;$

Check

Show answer

Forgetting to include all inputs of combinational logic in the always procedure's sensitivity list is a common error. While the procedure is legal Verilog, the procedure does not describe combinational logic.

#### PARTICIPATION ACTIVITY

3.25.6: Detect the error in defining a module for combinational logic.

Click the erroneous code.

```
1) module CloseDoor(a, b, c, z);
    input a, b, c;
    output reg z;
    always @ (a, b) begin
        z = ~a | ~b | ~c;
    end
endmodule
```

```
2) module SoundAlarm(a, b, y, z);
```

```
input a, b;  
output reg y, z;  
always @(a, b)  
    y = a & b;  
    z = a;  
endmodule
```

3) module LightController(a, b, z);  
 input a, b;  
 output z;  
 always @(a, b) begin  
 z = a | b;  
 end  
endmodule

4) module UnlockDoor(y, z, c, d);  
 input c, d;  
 output reg y, z;  
 always @(c, d) begin  
 y = ~c;  
 z = c ^ d;  
 end  
end module

5) module StartEngine(a, b, z)  
 input a, b;  
 output reg z;  
 always @(a, b) begin  
 z = ~(a & b);  
 end  
endmodule



PARTICIPATION  
ACTIVITY

## 3.25.7: HDL simulator: Always procedure.

Start ☐ 2x speed


```

module DoorOpenDetector(b, c, z);
  input b, c;
  output reg z;

  always @(b, c) begin
    z = b & ~c;
  end
endmodule

```

Timing diagram

 PARTICIPATION  
ACTIVITY

## 3.25.8: Combinational logic simulator: Designer provides input values; running the simulator generates output values.

```

module CombinationalLogicExample(a, b, c, z);
  input a, b, c;
  output reg z;
  always @(a, b, c) begin
    z = a & b & c;
  end
endmodule

```

Inputs: *click waveform to edit*

Run

Output:


**PARTICIPATION  
ACTIVITY**

## 3.25.9: Sensitivity list.


```

module AirController(h, j, k, y);
  input h, j, k;
  output reg y;

  always@(h, j, k) begin
    y = h | (~j & k);
  end
endmodule

```

Timing diagram

 

- 1) Value of y at (a).
  - ☐ 0
  - ☐ 1
- 2) The always procedure executes at 30 ns.
  - ☐ True
  - ☐ False
- 3) Value of y at (b).
  - ☐ 0
  - ☐ 1
- 4) The always procedure executes at 50 ns.
  - ☐ True
  - ☐ False
- 5) Value of y at (c).
  - ☐ 0
  - ☐ 1

 **Provide feedback on this section**