

7.9 Multi-function registers

A designer commonly wants to **clear** a register, meaning to load 0's. Registers commonly come with a control input named register with clear and load control inputs can be implemented using 4x1 muxes. A register with multiple functions, like clear, is called a **multi-function register**.

PARTICIPATION
ACTIVITY

7.9.1: Multi-function register with load and clear.

Start ☐ 2x speed

Note: clk connections with FF clk inputs are not shown.

d2

0

i3 i2 i1 i0

s1 4x1

s0 y

d

D FF

q

3-bit multi-function
register

q2

d1

0

i3 i2 i1 i0

s1 4x1

s0 y

d

D FF

q

q1

d0

0

i3 i2 i1 i0

s1 4x1

s0 y

d

D FF

q

q0

Function table

| clr | ld | Register function |
|-----|----|-------------------|
| 0 | 0 | Maintain |
| 0 | 1 | Load |
| 1 | 0 | Clear |
| 1 | 1 | Maintain |

Block symbol

3

clr D

ld 3-bit multi-function register

Q

3


<https://learn.zybooks.com/zybook/FIUCDA3103CickovskiFall2018/chapter/7/section/9>

1/7

PARTICIPATION
ACTIVITY

 7.9.2: Trace a register's behavior: Load and clear.

For the given values of D, clr, ld, and clk, indicate the register's Q value.



1) (a)

Q =

Check [Show answer](#)

2) (b)

Q =

Check [Show answer](#)

3) (c)

Q =

Check [Show answer](#)

4) (d)

Q =

Check Show answer


A **shift register** shifts contents by one position, shifting in a new bit too. Ex: A 4-bit right-shift register holding 1100 become shift, assuming the shifted-in bit is 0; the rightmost bit (0) is discarded.

PARTICIPATION
ACTIVITY

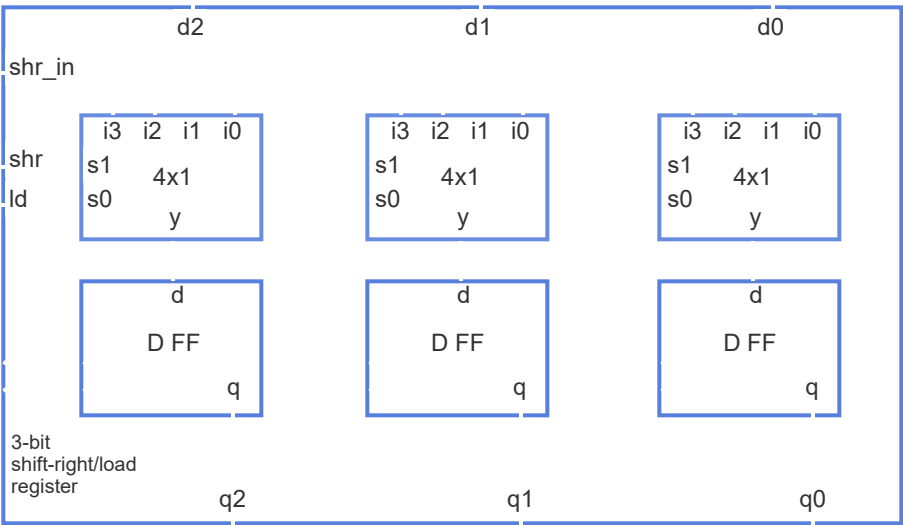7.9.3: A register with shift-right and load.

Start ☐ 2x speed


Note: clk connections with FF clk inputs are not shown.



Function table

| shr | ld | Register function |
|-----|----|-------------------|
| 0 | 0 | Maintain |
| 0 | 1 | Load |
| 1 | 0 | Shift-right |
| 1 | 1 | Maintain |

Block symbol

 

PARTICIPATION
ACTIVITY

7.9.4: Register with shift right and load.

For the given values of D, shr, shr_in, ld, and clk, indicate the register's Q value.

- 1) D is 111, shr_in is 0, shr is 0, ld is 0, and Q is 101.
clk rises. What does Q become?

Check [Show answer](#)

- 2) D is 111, shr_in is 0, shr is 0, ld is 1, and Q is 101.
clk rises. What does Q become?

Check [Show answer](#)

- 3) D is 111, shr_in is 0, shr is 1, ld is 0, and Q is 101.
clk rises. What does Q become?

Check [Show answer](#)


- 4) D is 111, shr_in is 1, shr is 1, ld is 0, and Q is 101.
clk rises. What does Q become?

Check [Show answer](#)

PARTICIPATION ACTIVITY

 7.9.5: Register with load, clear, and increment.

Note: clk connections with FF clk inputs are not shown




| inc | clr | ld | s1 | s0 | Register function |
|-----|-----|----|----|----|-------------------|
| 0 | 0 | 0 | 0 | 0 | Maintain |
| 0 | 0 | 1 | 0 | 1 | Load |
| 0 | 1 | 0 | 1 | 0 | Clear |
| 0 | 1 | 1 | 0 | 0 | (Maintain) |
| 1 | 0 | 0 | 1 | 1 | Increment |
| 1 | 0 | 1 | 0 | 0 | (Maintain) |
| 1 | 1 | 0 | 0 | 0 | (Maintain) |
| 1 | 1 | 1 | 0 | 0 | (Maintain) |

$$s1 = inc' \cdot clr \cdot ld' + inc \cdot clr' \cdot ld'$$

$$s_0 = \text{inc}' \cdot \text{clr}' \cdot \text{ld} + \text{inc} \cdot \text{clr}' \cdot \text{ld}'$$

**PARTICIPATION
ACTIVITY**

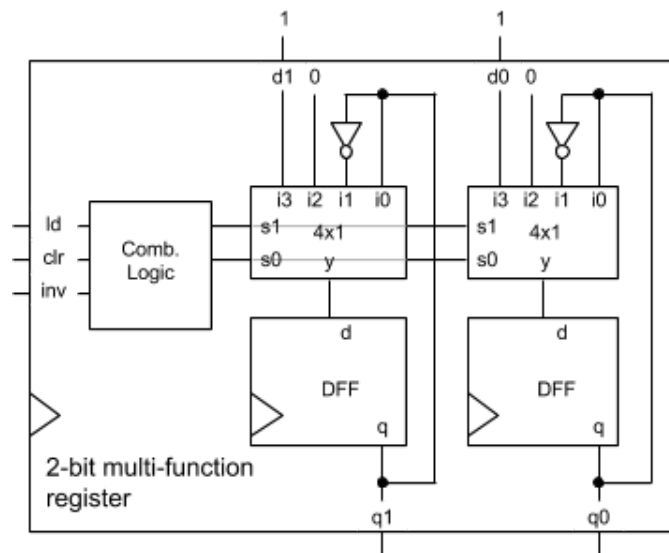7.9.6: Multi-function registers: Load, clear, invert.



| ld | clr | inv | s1 | s0 | Register function |
|----|-----|-----|-----|----|-------------------|
| 0 | 0 | 0 | 0 | 0 | Maintain |
| 0 | 0 | 1 | (F) | | Invert bits |
| 0 | 1 | 0 | (G) | | Clear |
| 0 | 1 | 1 | 0 | 0 | (Maintain) |
| 1 | 0 | 0 | (H) | | Load |
| 1 | 0 | 1 | 0 | 0 | (Maintain) |
| 1 | 1 | 0 | 0 | 0 | (Maintain) |
| 1 | 1 | 1 | 0 | 0 | (Maintain) |

1) (F)

- ☐ $s1s0 = 00$
☐ $s1s0 = 01$
☐ $s1s0 = 10$

2) (G)

- ☐ $s1s0 = 00$
☐ $s1s0 = 10$
☐ $s1s0 = 11$

3) (H)

- ☐ $s1s0 = 11$
☐ $s1s0 = 10$

☐ $s1s0 = 01$



Provide feedback on this section