

## 7.7 D flip-flops and registers

### D latch


A **D latch** stores one bit, with an input  $d$  having the bit to be stored, an input  $e$  that when 1 enables storing the bit, and with  $t$  appearing on output  $q$ .  $D$  and  $d$  are short for "data", and  $e$  for "enable".

An SR latch has an oscillation problem if both inputs were 1's then both change back to 0's. A D latch can be implemented SR latch with  $s = d$  and  $r = d'$ . Because  $sr = 11$  is impossible, the SR latch oscillation problem is avoided. When  $e = 1$ , the AND to  $s$ , and  $d'$  to  $r$ . So  $d = 1$  sets the SR latch, and  $d = 0$  resets. When  $e = 0$ , the AND gates pass 0's to  $s$  and  $r$ , so the SR latch  $n$  stored bit.

#### PARTICIPATION ACTIVITY

#### 7.7.1: D latch.

Start ☐ 2x speed

 

0

Figure 7.7.1: D latch behavior.

e	d	q
0	0	Previously-stored bit (d is ignored)
0	1	Previously-stored bit (d is ignored)
1	0	0 (d is stored)
1	1	1 (d is stored)

**PARTICIPATION  
ACTIVITY**

## 7.7.2: D latch.

Indicate q's present value for the given input sequence. "d: 0..1" means d was 0 and is presently 1.

1) d: 0

e: 1

☐ 1☐ 0

2) d: 0..0

e: 1..0

☐ 1☐ 0

3) d: 0..0..1

e: 1..0..0

☐ 1☐ 0

4) d: 0..0..1..1

e: 1..0..0..1

☐ 1☐ 0

5) d: 0..0..1..1..0

e: 1..0..0..1..0

☐ 1☐ 0

## Clock

For reasons that will be clear in later sections relating to synchronizing bit storage in a circuit, most digital circuits use a reg signal, called a **clock** signal, to control when to store bits. Ex: A clock signal may oscillate at a frequency of 1 GHz (1 billion second). Rather than bits being stored while an enable signal is high, bits are stored only at the instant a clock signal changes known as a **rising edge**.

### PARTICIPATION ACTIVITY

7.7.3: Clocking synchronizes components.

Start ☐ 2x speedclk  
1  
0

Bit storage



0 0 1 1

**PARTICIPATION  
ACTIVITY**

## 7.7.4: Clocks.

Consider the example above.

- 1) A change of the clock signal from 0 to 1 is called a rising \_\_\_\_ .
  - ☐ edge
  - ☐ cliff
- 2) The three boxes represent three stored bits. On each rising clock edge, those bits move one place to the \_\_\_\_ .
  - ☐ left
  - ☐ right
- 3) On each rising clock edge, the bits move \_\_\_\_ .
  - ☐ one at a time
  - ☐ simultaneously

## D flip-flop

A ***latch*** stores a new bit while an enable input is 1. A latch is said to be ***level sensitive***, storing when the enable's "level" is high. A ***flip-flop*** stores a new bit only at the instant of an enable signal's rising edge. A flip-flop is said to be ***edge-triggered***.

**PARTICIPATION  
ACTIVITY**

## 7.7.5: D flip-flop.

Given a single D flip-flop with data input d, clock input clk, and output q.

- 1) d is 0, clk is 0, q is 0.  
d changes to 1. Moments later, what is q?  
☐ 1  
☐ 0
- 2) d is 0, clk is 0, q is 0.  
clk changes to 1. Moments later, what is q?  
☐ 1  
☐ 0
- 3) d is 0, clk is 0, q is 0.  
d changes to 1, then clk changes to 1.  
Moments later, what is q?  
☐ 1  
☐ 0
- 4) d is 1, clk is 0, q is 1.  
d changes to 0. Moments later, what is q?  
☐ 1  
☐ 0


A D flip-flop can be implemented by cascading two D latches, with the first latch's enable inverted. A flip-flop implemented with the first latch's enable inverted, has a **master-servant** arrangement. (Actually, master-slave is the common term, which

avoids for obvious reasons). The first latch is the master, the second the servant. Other implementations exist.

### PARTICIPATION ACTIVITY

#### 7.7.6: D flip-flop: Master-servant implementation.

Start ☐ 2x speed

 

### PARTICIPATION ACTIVITY

#### 7.7.7: D flip-flop implemented as master-servant.

Given a single D flip-flop implemented with a master-servant arrangement.

1) **d** is 0, **clk** is 0, **q** is 1.

What is in the first latch?

- ☐ 1  
☐ 0

2) **d** is 0, **clk** is 0, **q** is 1.

What is in the second latch?

- ☐ 1  
☐ 0

0

**CHALLENGE  
ACTIVITY**

7.7.1: Indicate q's value over time.


Start



s

r

q

 

1

2

3

4

Check


Next

**Basic register**

Bits are usually stored in groups. A **register** is a circuit that stores a group of bits; a 3-bit register stores three bits. On a rising edge of the clock, bits are stored simultaneously. Storing bits in a register is known as **loading** the register. A common register implementation

### PARTICIPATION ACTIVITY

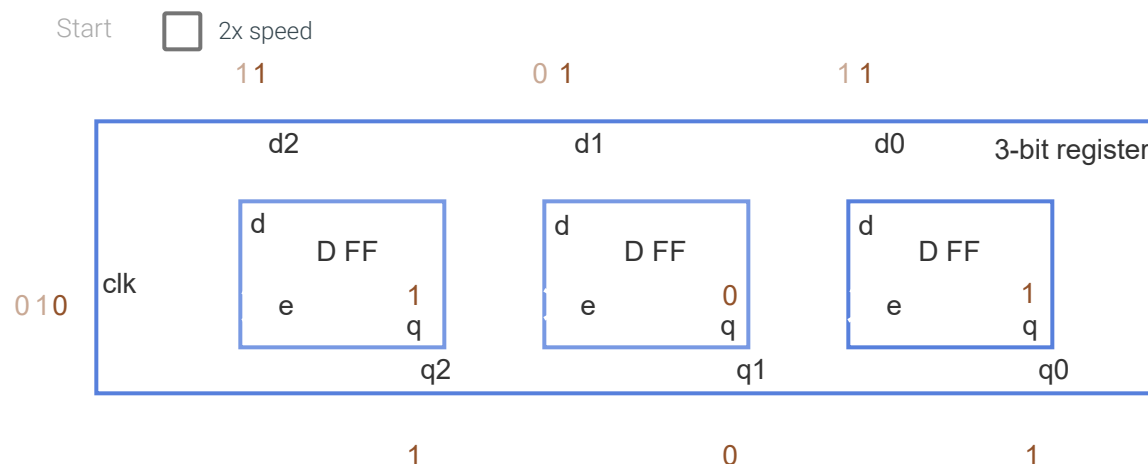7.7.8: 3-bit register using 3 flip-flops: Inputs only stored on rising clk.



### PARTICIPATION ACTIVITY

7.7.9: Basic register.

Given a 3-bit register with data inputs d2, d1, d0, clock input clk, and outputs q2, q1, q0.

- 1) d2d1d0 is 101, and q2q1q0 is 000.  
clk rises. What does q2q1q0 become?

Check

Show answer

- 2) d2d1d0 is 111, q2q1q0 is 000, clk rises



so  $q_2q_1q_0$  becomes 111.  
Then  $d_2d_1d_0$  changes to 010. What  
does  $q_2q_1q_0$  become?

[Check](#)[Show answer](#)[Provide feedback on this section](#)